

MbW Lathe — Raspberry Pi 4B Hardware Wiring Guide

Target hardware: Raspberry Pi 4B · ClearPath SDSK servos · CUI AMT103-V encoders · AutoTech C3 spindle sensor

GPIO numbering: BCM throughout

Signal voltage: RPi GPIO = 3.3 V logic — level shifters **mandatory** for 5 V devices

Table of Contents

1. [Component List](#)
 2. [Power Rail Extraction](#)
 3. [System Overview Diagram](#)
 4. [Step-by-Step Connections](#)
 5. [Step 1 — Power Setup](#)
 6. [Step 2 — RPi + Touchscreen](#)
 7. [Step 3 — Z-Axis Encoder](#)
 8. [Step 4 — X-Axis Encoder](#)
 9. [Step 5 — Spindle Sensor + Voltage Divider](#)
 10. [Step 6 — Z-Axis Level Shifter + ClearPath Z](#)
 11. [Step 7 — X-Axis Level Shifter + ClearPath X](#)
 12. [Step 8 — ClearPath 70 V Motor Power](#)
 13. [Step 9 — ADS1115 ADC + Potentiometer](#)
 14. [Step 10 — Push Buttons \(×3\)](#)
 15. [Step 11 — Half-Nut Lever Switch](#)
 16. [Step 12 — Limit Switches \(×4\)](#)
 17. [Step 13 — E-Stop + Relay Module](#)
 18. [Final System Verification](#)
 19. [GPIO Quick Reference](#)
-

1. Component List

All items are available as off-the-shelf modules from common electronics retailers.

1.1 Core Processing

#	Component	Model / Spec	Qty	Source
1	Raspberry Pi 4B (4 GB)	RPi 4 Model B	1	raspberrypi.com, Adafruit, PiShop
2	microSD Card (32 GB A1)	Samsung Endurance Pro	1	Amazon
3	RPi USB-C Power Supply	Official 5.1 V / 3 A	1	raspberrypi.com
4	7" HDMI Capacitive Touchscreen	Elecrow 800×480 or equiv.	1	Amazon, Elecrow

1.2 Motion & Sensing

#	Component	Model / Spec	Qty	Notes
5	Handwheel Encoder	CUI AMT103-V	2	2000 CPR, 3.3 V compatible
6	Encoder Cable	CUI 435-1FT	2	5-pin MTA-100 connector
7	ClearPath Servo (Z-Axis)	Teknic SDSK	1	Existing — 800 counts/rev in MSP
8	ClearPath Servo (X-Axis)	Teknic SDSK	1	Same as Z
9	Servo Signal Cable	Teknic CPM-CABLE-CTRL-MU120	2	8-pin Molex Mini-Fit, one per motor
10	Servo Power Cable	Teknic CPM-CABLE-PWR-MS120	2	One per motor

11	Spindle Index Card + Sensor	AutoTech C3	1	5 V TTL output, single-hole optical
----	-----------------------------	-------------	---	-------------------------------------

1.3 Signal Conditioning

#	Component	Model / Spec	Qty	Notes
12	Bidirectional Level Shifter	TXS0108E Module (8-channel)	2	One per servo axis (3.3 V → 5 V). Uses 3 of 8 channels per module.
13	ADC Module	Adafruit ADS1115	1	16-bit, I2C, 3.3 V
14	10 kΩ Resistor (1/4 W)	Through-hole	10	Pull-ups, pull-downs, V-divider
15	20 kΩ Resistor (1/4 W)	Through-hole	2	Spindle voltage divider lower leg

1.4 User Inputs

These are the operator controls read directly by the RPi GPIO. All are defined in `config.py`.

#	Component	Model / Spec	Qty	Notes
16	Potentiometer (10 kΩ linear)	Bourns 3547S or equiv.	1	Feed-rate knob → ADS1115 A0

17	Momentary Push Button (NO)	2-pin panel mount	3	Memory / Zero / Units (GPIO 26/20/21)
18	Half-Nut Lever Microswitch	Omron D2HW-C213MR or equiv.	1	Lever-actuated NO contact (GPIO 4)
19	Limit Switch (NO)	Generic panel mount	4	Z+/Z-/X+/X- (GPIO 16/7/8/11)

1.5 Safety

Hard-wire E-Stop path. The relay is controlled directly by the physical button — no GPIO line required from the RPi.

#	Component	Model / Spec	Qty	Notes
20	E-Stop Button (40 mm mushroom)	Latching NC/NO combo	1	ABB / Schneider / Idec preferred
21	2-Channel 5 V Relay Module	Optocoupler-isolated, JD-VCC type	1	Hard-cuts ClearPath ENABLE line

1.6 Power & Wiring

#	Component	Model / Spec	Qty	Notes
22	70 V DC Power Supply	Generic, ≥ 7 A	1	Servo bus power
23	DC-DC Buck Converter Module	LM2596 adjustable or XL4016	1	Set to 5 V — for C3 sensor + relay


[illegible]

Ground rule: All GNDs in this system must be tied to a single common ground bus — RPi GND, buck module GND, 70 V PSU GND. Floating grounds cause erratic signals.

2.3 Power Budget Summary

Consumer	Supply	Est. Current
RPi 4B (idle)	USB-C 5.1 V / 3 A PSU	~600 mA
7" Touchscreen (via USB)	USB from RPi	~500 mA
Z Encoder (AMT103-V)	3.3 V header	~20 mA
X Encoder (AMT103-V)	3.3 V header	~20 mA
ADS1115 ADC	3.3 V header	<1 mA
Level Shifter Z — VCCA	3.3 V header	~2 mA
Level Shifter X — VCCA	3.3 V header	~2 mA
Level Shifter Z — VCCB	5 V (GPIO Pin 2)	~2 mA
Level Shifter X — VCCB	5 V (GPIO Pin 2)	~2 mA
AutoTech C3 sensor	5 V (buck module)	~50 mA
Relay module (2-ch)	5 V (buck module)	~80 mA
ClearPath Z + X servos	70 V DC	≤7 A peak

3. System Overview Diagram

 

4. Step-by-Step Connections

Safety rule: Power off **all** supplies before making or changing any wiring. Only power up during the verification steps.

Step 1 — Power Setup

Parts needed: RPi USB-C PSU, 70 V DC PSU, LM2596 buck module, mains power strip with switch, multimeter.

1a. Adjust Buck Module (do this before connecting any load)

1. Connect buck IN+ to 70 V PSU terminal +
2. Connect buck IN- to 70 V PSU terminal - (GND)
3. Power ON the 70 V PSU (nothing else connected)
4. Measure VOUT with multimeter – trim potentiometer until VOUT = 5.00 V
5. Power OFF. Wait 30 s for capacitors to discharge.

1b. Common Ground Bus

All grounds must be connected together. Use a 3-position terminal block on DIN rail as the GND bus.

```
70 V PSU GND ■■■ Buck GND ■■■■■■■■■■■ Common GND Bus (terminal block) ■■■■ RPi
GND (Pin 6 / 9 / 14) RPi PSU GND ■■■■
```

Verification — Step 1

Test	Expected Result	Tool
Buck VOUT (no load)	5.00 V $\pm$ 0.05 V	Multimeter
70 V PSU output	68–72 V	Multimeter
GND continuity bus-to-bus	< 1 Ω	Continuity mode

Step 2 — RPi + Touchscreen

Parts needed: Raspberry Pi 4B, microSD with OS flashed, USB-C PSU, 7" HDMI touchscreen.

Wiring

Use a micro-HDMI to full-HDMI cable. RPi 4 has **micro-HDMI** (not mini-HDMI).

Verification — Step 2

Test	Expected Result
------	-----------------

RPi powers on	Red LED on, green LED activity
Touchscreen displays RPi desktop	800×480, no artefacts
Touch input responds	Cursor moves, tap registers

Step 3 — Z-Axis Encoder (CUI AMT103-V)


Parts needed: CUI AMT103-V encoder, CUI 435-1FT cable.

The AMT103-V operates at 3.3 V and is directly compatible with RPi GPIO — no level shifter needed.

Wiring

AMT103-V → Raspberry Pi 4B

Pin 1 (VCC)	3.3 V (Pin 1)	Pin 2 (GND)	GND (Pin 6)	Pin 5 (A)	GPIO 5 (Pin 29)	Pin 6 (B)	GPIO 6 (Pin 31)	Pin 3/4 (IDX)	Not connected
-------------	---------------	-------------	-------------	-----------	-----------------	-----------	-----------------	---------------	---------------

 

Verification — Step 3

```
# Run on RPi – test Z encoder (requires pigpiod running)
import pigpio, time
pi = pigpio.pi()
pi.set_mode(5, pigpio.INPUT)
pi.set_mode(6, pigpio.INPUT)
pi.set_pull_up_down(5, pigpio.PUD_UP)
pi.set_pull_up_down(6, pigpio.PUD_UP)
```

```
print("Rotate Z handwheel. GPIO 5 and 6 should toggle.") for _ in range(30):
print(f" A={pi.read(5)} B={pi.read(6)}", end='\r') time.sleep(0.1) pi.stop()
```

Test	Expected Result
GPIO 5 reads 1 at rest	Internal pull-up active
GPIO 5 and 6 toggle on rotation	Quadrature signal present
A leads B on CW rotation	Phase relationship correct


Step 4 — X-Axis Encoder (CUI AMT103-V)

Parts needed: Second CUI AMT103-V encoder, CUI 435-1FT cable.

Identical wiring to Step 3 — uses GPIO 13 (A) and GPIO 19 (B).

Wiring
 
```
AMT103-V → Raspberry Pi 4B Pin 1 (VCC) 3.3 V (Pin 17) Pin 2 (GND) GND (Pin 9) Pin 5 (A) GPIO 13 (Pin 33) Pin 6 (B) GPIO 19 (Pin 35) Pin 3/4 (IDX) Not connected
```



Verification — Step 4

```
import pigpio, time
pi = pigpio.pi()
pi.set_mode(13, pigpio.INPUT)
pi.set_mode(19, pigpio.INPUT)
pi.set_pull_up_down(13, pigpio.PUD_UP)
pi.set_pull_up_down(19, pigpio.PUD_UP)
print("Rotate X handwheel. GPIO 13 and 19 should toggle.")
for _ in range(30):
    print(f" A={pi.read(13)} B={pi.read(19)}", end='\r')
    time.sleep(0.1)
pi.stop()
```


Step 5 — Spindle Sensor + Voltage Divider

Parts needed: AutoTech C3 card + optical sensor, 10 k Ω resistor (R1), 20 k Ω resistor (R2), small breadboard.

■ **Mandatory:** The C3 outputs **5 V TTL**. RPi GPIO maximum input is **3.3 V**. A voltage divider is required.

Voltage Divider Circuit

Full C3 Wiring

 

Verification — Step 5

```
import pigpio, time pi = pigpio.pi() pulse_count = [0] def on_pulse(gpio, level,
tick): pulse_count[0] += 1 pi.set_mode(12, pigpio.INPUT) pi.callback(12,
pigpio.RISING_EDGE, on_pulse) print("Rotate spindle slowly by hand. Count
increments once per revolution.") start = time.time() while time.time() - start <
15: print(f" Pulses: {pulse_count[0]}", end='\r') time.sleep(0.1) pi.stop()
```

Test	Expected Result	Tool
------	-----------------	------

Voltage at junction node	3.30–3.36 V	Multimeter
GPIO 12 level between pulses	0 (low)	Script above
Pulses per spindle revolution	Exactly 1	Script above

Step 6 — Z-Axis Level Converter + ClearPath Z Servo


Parts needed: 4-Channel Logic Level Converter module ×1, ClearPath Z signal cable (CPM-CABLE-CTRL-MU120).

■ **Mandatory:** RPi outputs 3.3 V logic; ClearPath STEP / DIR / ENABLE require 5 V TTL. The level converter shifts all three signals. Only 3 of the 4 channels are used — 1 channel spare.

Level Converter Wiring — Z Axis

RPi (3.3 V side – LV) 4-Ch Level Converter ClearPath Z (5 V side – HV)

 GPIO 17 (Z STEP) LV1 HV1 STEP
input GPIO 27 (Z DIR) LV2 HV2 DIR input GPIO 22 (Z EN) LV3 HV3
HV3 ENABLE input (via relay NC, Step 13) 3.3 V (Pin 1) LV (ref) HV
5 V (GPIO Pin 2) GND GND GND



ClearPath SDK Signal Connector (8-pin Molex Mini-Fit)

Verification — Step 6

Test	Expected Result	Tool
VCCA on TXS0108E	3.3 V	Multimeter
VCCB on TXS0108E	5.0 V	Multimeter
B1 / B2 / B3 when RPi drives HIGH	4.8–5.0 V	Multimeter
B1 / B2 / B3 when RPi drives LOW	0 V	Multimeter

Parts needed: TXS0108E module ×1, ClearPath X signal cable.

Level Shifter Wiring — X Axis

```
input (via relay NC, Step 13) 3.3 V (Pin 17) ■■■■■■ VCCA VCCB ■■■■ 5 V (GPIO Pin
4) GND ■■■■■■ GND GND OE pin ■■■■■■ Tie to VCCA (always enabled)
```

Verification — Step 7

Same test as Step 6 — substitute GPIO 23 / 24 / 25 and the second TXS0108E module.


Step 8 — ClearPath 70 V Motor Power

Parts needed: 70 V DC PSU (already set up in Step 1), Teknic CPM-CABLE-PWR-MS120 (x2).

■ **High voltage.** The 70 V bus is hazardous. Verify all connections are insulated before powering up. Motors must be mechanically secured.

Wiring

 Wire gauge: Use minimum 16 AWG for the 70 V bus wires.



Verification — Step 8

Test	Expected Result	Tool
70 V PSU output under no load	68–72 V	Multimeter
No motor movement at power-up	Correct — motors are inactive until ENABLE + STEP are driven	Visual
ClearPath HLFEB LED (after ENABLE assertion)	Solid green = ready	Visual

Step 9 — ADS1115 ADC + Potentiometer

Parts needed: Adafruit ADS1115 module, 10 kΩ linear potentiometer.

The RPi has no onboard ADC. The ADS1115 provides 16-bit analog-to-digital conversion over I2C for the feed-rate potentiometer.


I2C Wiring (ADS1115)

ADS1115 Module → Raspberry Pi 4B
VDD 3.3 V (Pin 1) GND GND (Pin 6) SDA GPIO 2 / SDA (Pin 3) SCL
GPIO 3 / SCL (Pin 5) ADDR GND → sets I2C address to 0x48 ALRT Not
connected

Potentiometer Wiring

Potentiometer → Destination End A
(CCW stop) GND Wiper (centre) ADS1115 A0 input End B (CW stop)
3.3 V

 Use 3.3 V (not 5 V) to power the pot ends. The ADS1115 A0 input maximum is VDD = 3.3 V.



Verification — Step 9

```
# Enable I2C on RPi (once) sudo raspi-config # Interface Options → I2C → Enable
sudo reboot # Scan for ADS1115 on the I2C bus sudo apt install -y i2c-tools
i2cdetect -y 1 # Expected: "48" appears at address 0x48
```

```
import board, busio from adafruit_ads1x15.ads1115 import ADS1115 from
adafruit_ads1x15.analog_in import AnalogIn i2c = busio.I2C(board.SCL, board.SDA)
ads = ADS1115(i2c) chan = AnalogIn(ads, 0) # A0 channel print(f"Voltage:
{chan.voltage:.3f} V") # Rotate pot fully CW → ~3.3 V; fully CCW → ~0.0 V
```

Test	Expected Result
i2cdetect output	Address 0x48 visible
Pot at minimum (CCW)	~0.0 V
Pot at maximum (CW)	~3.3 V
Pot at midpoint	~1.65 V

Step 10 — Push Buttons (×3)


Parts needed: Momentary push buttons ×3 (NO, 2-pin).

GPIO internal pull-up is used. Buttons are **active LOW** — pressed = 0 V, released = 3.3 V.

Wiring (per button)

GPIO pin ■■■■■■■■■■ Button terminal A Button terminal B ■■■■■ GND No external resistor needed – RPi internal pull-up is enabled in software.

Button	Function	GPIO (BCM)	Physical Pin
Button 1	X Memory / Zero	GPIO 26	Pin 37
Button 2	Z Memory / Zero	GPIO 20	Pin 38
Button 3	Units / Stop	GPIO 21	Pin 40

 

Verification — Step 10


```
import pigpio, time
pi = pigpio.pi()
for pin in [26, 20, 21]: pi.set_mode(pin, pigpio.INPUT)
pi.set_pull_up_down(pin, pigpio.PUD_UP)
print("Press each button. Its value should drop to 0.")
for _ in range(40):
    print(f" BTN1={pi.read(26)} BTN2={pi.read(20)} BTN3={pi.read(21)}", end='\r')
    time.sleep(0.2)
pi.stop()
```

Step 11 — Half-Nut Lever Switch

Parts needed: Lever microswitch (Omron D2HW-C213MR or equivalent), 10 kΩ resistor (pull-down).

This switch is **active HIGH** — lever engaged = 3.3 V, lever released = 0 V.

Wiring

 

Verification — Step 11

```
import pigpio, time
pi = pigpio.pi()
pi.set_mode(4, pigpio.INPUT)
pi.set_pull_up_down(4, pigpio.PUD_DOWN)
print("Engage half-nut lever. GPIO 4 should read 1.")
for _ in range(25):
    print(f" Half-Nut = {pi.read(4)}", end='\r')
    time.sleep(0.2)
pi.stop()
```

Step 12 — Limit Switches (×4)

Parts needed: Normally Open (NO) panel-mount switches ×4.

GPIO internal pull-up is used. Switches are **active LOW** — triggered = 0 V.

Wiring (per limit switch)

GPIO pin


Switch terminal A

Switch terminal B

GND

No external resistor needed – RPi internal pull-up is enabled in software.

Axis	Position	GPIO (BCM)	Physical Pin
Z+	Far travel end	GPIO 16	Pin 36
Z–	Home / near end	GPIO 7	Pin 26
X+	Far travel end	GPIO 8	Pin 24
X–	Home / near end	GPIO 11	Pin 23

 

Verification — Step 12

```
import pigpio, time
pi = pigpio.pi()
for pin in [16, 7, 8, 11]: pi.set_mode(pin, pigpio.INPUT)
pi.set_pull_up_down(pin, pigpio.PUD_UP)
print("Trigger each limit switch. Its value should drop to 0.")
for _ in range(40):
    print(f" Z+={pi.read(16)} Z-={pi.read(7)} X+={pi.read(8)} X-={pi.read(11)}", end='\r')
    time.sleep(0.2)
pi.stop()
```

Step 13 — E-Stop + Relay Module

Parts needed: Latching NC/NO E-Stop mushroom button (40 mm), 2-channel 5 V optocoupler relay module (JD-VCC isolated type).

The E-Stop is a **purely hardware circuit** — the relay is driven directly by the physical button's NC contact. No RPi GPIO pin is required. This is the correct fail-safe design: software cannot prevent or delay the ENABLE cut.

Fail-safe principle: When the E-Stop NC contact breaks (button pressed), the relay de-energises, NC contacts open, and ClearPath ENABLE drops to 0 V — even if the RPi is frozen or unpowered.

How It Works

Most common relay modules are active-LOW: IN1 LOW = relay energised = NC closed.
Normal operation (E-Stop NOT pressed): NC contact closed → IN1 pulled to GND →

```

relay ON → NC contacts CLOSED → 5 V reaches ClearPath ENABLE → servos can run
E-Stop PRESSED (mushroom latched in): NC contact opens → 10 kΩ pulls IN1 HIGH →
relay OFF → NC contacts OPEN → ENABLE line cut → both ClearPath servos
immediately stop

```

Wiring

[illegible]

2-Ch Relay Module → Destination

VCC (coil supply) 5 V (buck module) GND Common GND JD-VCC (isolated)
5 V (buck module) ← keep isolated from VCC IN1 (CH1 trigger) E-Stop NC
circuit (see schematic below) IN2 (CH2 trigger) Tied to IN1 (both channels
trip together) COM1 5 V (buck module) ← ENABLE supply rail NC1
ClearPath Z ENABLE (→ Level Converter B3) COM2 5 V (buck module) NC2
ClearPath X ENABLE (→ Level Converter B3)


E-Stop Button → Relay Trigger Circuit

5 V (buck) ■■■■ 10 kΩ ■■■■■■■■■■ Relay IN1 / IN2 ■ E-Stop NC contact ■ GND NC
closed (not pressed): IN1 = 0 V → relay ON → NC contacts CLOSED → ENABLE = 5 V NC
open (pressed): IN1 = 5 V → relay OFF → NC contacts OPEN → ENABLE = 0 V

■ If your relay module is **active-HIGH** (less common), swap the logic: connect 5V through NC to IN1, and use a pull-down to GND instead.

Complete E-Stop Schematic
 
```
Buck 5V 10 kΩ IN1 (active-LOW trigger) E-Stop NC contact
GND COM1 Relay NC1 ClearPath Z ENABLE Level
Converter B3 COM2 Relay NC2 ClearPath X ENABLE Level
Converter B3
```



Verification — Step 13

Test	Expected Result	Tool
E-Stop NOT pressed — ENABLE voltage at ClearPath	~5 V (relay NC closed)	Multimeter

E-Stop PRESSED — ENABLE voltage at ClearPath	0 V (relay NC open)	Multimeter
Relay click audible on press	Yes — both channels	Audible
ClearPath HLFB LED on ENABLE cut	Amber / off (servo disabled)	Visual

5. Final System Verification

5.1 Pre-Power Checklist

- ☐ All GNDs tied to common ground bus
- ☐ Buck module output verified at 5.00 V before connecting any load
- ☐ No exposed wire ends contacting adjacent conductors
- ☐ Level shifter VCCA = 3.3 V, VCCB = 5 V verified (Steps 6 and 7)
- ☐ Spindle voltage divider output verified at ≤ 3.36 V (Step 5)
- ☐ ClearPath motors mechanically secured before applying 70 V
- ☐ E-Stop relay tested and ENABLE line confirmed cut on press (Step 13)

5.2 Full GPIO State Scan

```
# Run before starting the lathe application – confirms all pins are reachable
import pigpio PIN_MAP = { "Z Enc A": (5, "IN", pigpio.PUD_UP), "Z Enc B": (6, "IN",
pigpio.PUD_UP), "X Enc A": (13, "IN", pigpio.PUD_UP), "X Enc B": (19, "IN",
pigpio.PUD_UP), "Spindle": (12, "IN", pigpio.PUD_DOWN), "Z STEP": (17, "OUT",
None), "Z DIR": (27, "OUT", None), "Z ENABLE": (22, "OUT", None), "X STEP": (23,
"OUT", None), "X DIR": (24, "OUT", None), "X ENABLE": (25, "OUT", None), # Note:
E-Stop relay is purely hardware-driven (button NC → relay IN1). # No RPi GPIO pin
is assigned to E-Stop in config.py. "Button 1": (26, "IN", pigpio.PUD_UP), "Button
2": (20, "IN", pigpio.PUD_UP), "Button 3": (21, "IN", pigpio.PUD_UP), "Half-Nut":
(4, "IN", pigpio.PUD_DOWN), "Limit Z+": (16, "IN", pigpio.PUD_UP), "Limit Z-": (7,
"IN", pigpio.PUD_UP), "Limit X+": (8, "IN", pigpio.PUD_UP), "Limit X-": (11, "IN",
pigpio.PUD_UP), } pi = pigpio.pi() print(f"{'Signal':<14} {'GPIO':>5} {'Level'}")
print("-" * 32) for name, (pin, direction, pud) in PIN_MAP.items(): if direction ==
"IN": pi.set_mode(pin, pigpio.INPUT) pi.set_pull_up_down(pin, pud) level =
pi.read(pin) print(f"{'name':<14} GPIO {pin:<3} {level}") else: pi.set_mode(pin,
pigpio.OUTPUT) pi.write(pin, 0) print(f"{'name':<14} GPIO {pin:<3} [OUTPUT]")
pi.stop()
```

5.3 I2C Bus Scan

```
i2cdetect -y 1 # Expected: address 0x48 (ADS1115) is present on the bus
```

5.4 First Motion Test (Low-Speed Jog)

Complete all above steps and verifications first, then:

1. Connect a multimeter to ClearPath Z ENABLE line — confirm it reads 5 V (relay closed, E-Stop not pressed).
2. Launch the application: `python3 main.py --windowed`
3. Keep E-Stop button within arm's reach at all times.
4. Enable Z servo: software asserts GPIO 22 HIGH (via level shifter → ClearPath ENABLE HIGH).
5. Rotate Z handwheel slowly — Z carriage should track smoothly.
6. Test E-Stop: press the mushroom button — motor must stop immediately and ENABLE voltage drops to 0 V.
7. Release E-Stop (twist to unlatch) and repeat for X axis.

GPIO Quick Reference

[illegible]

```

##### Phys
BCM ■ Signal ■
##### 1 ■ 3.3
V ■ Power – Encoders, ADS1115 ■ ■ 2 ■ 5 V ■ Power – Level Shifter VCCB ■ ■ 3 ■
GPIO 2 (SDA) ■ I2C SDA → ADS1115 ■ ■ 4 ■ 5 V ■ Power – Level Shifter VCCB ■ ■ 5 ■
GPIO 3 (SCL) ■ I2C SCL → ADS1115 ■ ■ 6 ■ GND ■ Ground ■ ■ 7 ■ GPIO 4 ■ Half-Nut
lever switch ■ ■ 11 ■ GPIO 17 ■ Z STEP → LS-Z A1 ■ ■ 13 ■ GPIO 27 ■ Z DIR → LS-Z
A2 ■ ■ 15 ■ GPIO 22 ■ Z ENABLE→ LS-Z A3 ■ ■ 16 ■ GPIO 23 ■ X STEP → LS-X A1 ■ ■
17 ■ 3.3 V ■ Power – Encoders (2nd tap) ■ ■ 18 ■ GPIO 24 ■ X DIR → LS-X A2 ■ ■ 22
■ GPIO 25 ■ X ENABLE→ LS-X A3 ■ ■ 23 ■ GPIO 11 ■ Limit X- ■ ■ 24 ■ GPIO 8 ■
Limit X+ ■ ■ 26 ■ GPIO 7 ■ Limit Z- ■ ■ 29 ■ GPIO 5 ■ Z Encoder A ■ ■ 31 ■ GPIO 6
■ Z Encoder B ■ ■ 32 ■ GPIO 12 ■ Spindle index (via V-div) ■ ■ 33 ■ GPIO 13 ■ X
Encoder A ■ ■ 35 ■ GPIO 19 ■ X Encoder B ■ ■ 36 ■ GPIO 16 ■ Limit Z+ ■ ■ 37 ■
GPIO 26 ■ Button 1 (X memory) ■ ■ 38 ■ GPIO 20 ■ Button 2 (Z memory) ■ ■ 40 ■
GPIO 21 ■ Button 3 (Units / stop) ■ ■ 6/9 ■ GND ■ Ground (use all GND pins) ■
##### LS-Z =
TXS0108E Level Shifter (Z axis) LS-X = TXS0108E Level Shifter (X axis)

```